Staircase Wiring

Circuit diagram: 2 way switch SPDT

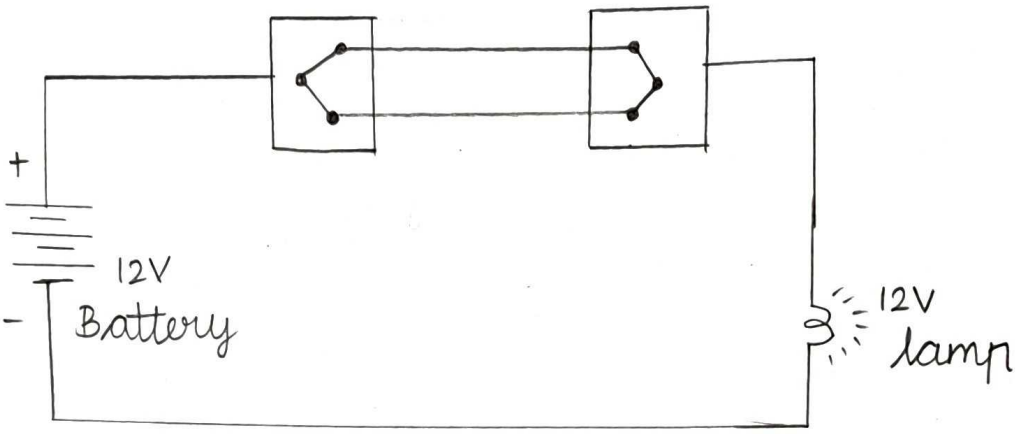

SPDT - single pole double throw switch

mode	S_1	S_2	Lamp
1	ON	ON	ON
2	ON	OFF	OFF
3	OFF	ON	OFF
4	OFF	OFF	ON

Components	Proteus	Specification
AC supply	Vsine	Amplitude 230V
Two way switch	SPDT	Frequency 50Hz
Lamp	Animated	230V

STAIRCASE WIRING

AIM:

To develop and test the staircase wiring using proteus.

APPARATUS REQUIRED:

Laptop with proteus software

SAVEETHA ENGINEERING COLLEGE SAVEETHA NAGAR 602 105

THEORY:

Staircase wiring is a common multiple way switching or two way switching connection. It involves wiring for one light with two switches. In this, setup is controlled by two switches located operate the load from seperate positions above or below the staircase from inside or outside of room or two way led switch.

Cross Connection

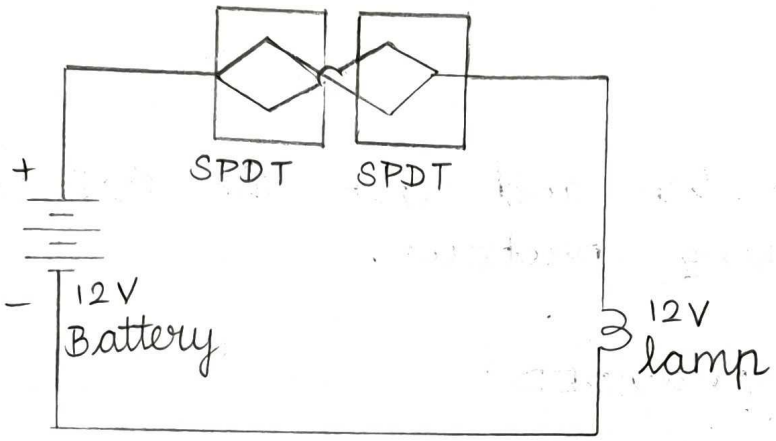

Mode	S_1	S_2	Lamp
1	ON	ON	OFF
2	ON	OFF	ON
3	OFF	ON	ON
4	OFF	OFF	OFF

PROCEDURE:

* Drag the required components from the process library.
* Connect the components as per the circuit diagram.
* Run the simulation and check the lamp for different switching condition.

SAVEETHA
ENGINEERING COLLEGE
SAVEETHA NAGAR 602 105
BE THE BEST
2001

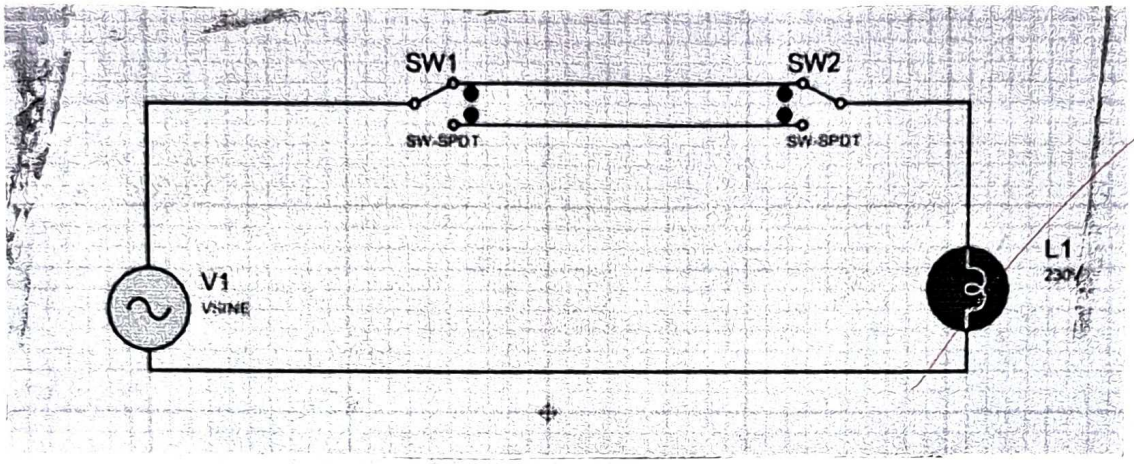
SW1
SW-SPDT
SW2
SW-SPDT
V1
VSINE
L1
230V

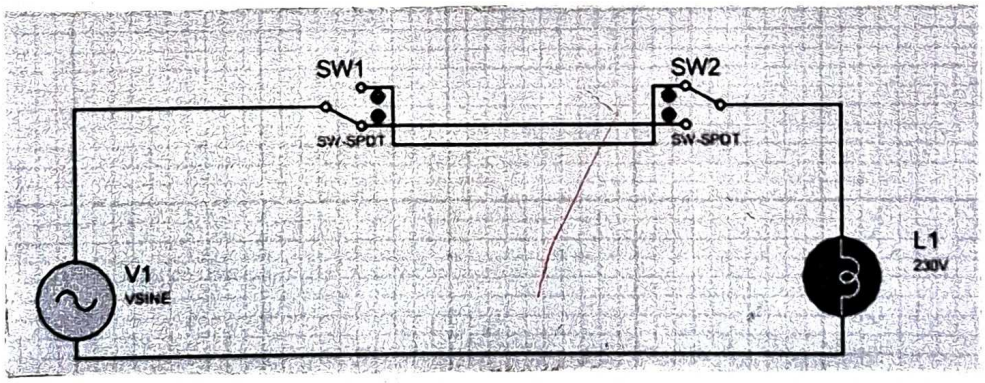
SW1
SW-SPDT
SW2
SW-SPDT
V1
VSINE
L1
230V

Expt. No.

SAVEETHA
ENGINEERING COLLEGE
SAVEETHA NAGAR 602 105
BE THE BEST

23/03/26

RESULT:

Thus the staircase using connection were developed and tested successfully.